



Signals passing through vertically are control inputs, and also vertical in the physical layout.

Right/left in/out signals are associated with the shift registers, and run vertically (but are not control)

4-bit bus outputs must take one bit from each bitslice and route them to the control unit above the datapath.