

 


The datapath is 338.4um wide and 76.7um long.

 
The area of the datapath is  $338.4 \times 76.7 = 25,955.28 \mu\text{m}^2$ .




 







 

 

 



 



si.out            Fri Apr 19 16:35:09 2019            1

@(#)SCDS: LVS version 6.1.7-64b 07/05/2016 20:10 (sjfhw313) \$

Command line: /software/cadence-Aug2016/IC617/tools.lnx86/dfII/bin/64bit/LVS -dir /home/grossfe2/ece425.work/LVS -l -s -t /home/grossfe2/ece425.work/LVS/layout /home/grossfe2/ece425.work/LVS/schematic

Like matching is enabled.

Net swapping is enabled.

Using terminal names as correspondence points.

```
Net-list summary for /home/grossfe2/ece425.work/LVS/layout/netlist
count
852          nets
86           terminals
928          pmos
928          nmos
```

```
Net-list summary for /home/grossfe2/ece425.work/LVS/schematic/netlist
count
852          nets
86           terminals
928          pmos
928          nmos
```

```
Terminal correspondence points
N801      N18      c<0>
N788      N62      c<1>
N782      N22      c<2>
N770      N52      c<3>
N839      N43      cin
N848      N10      d<0>
N834      N4       d<1>
N826      N57      d<2>
N815      N15      d<3>
N841      N40      f0_in
N812      N71      f3_in
N772      N34      f<0>
N849      N11      f<1>
N835      N29      f<2>
N827      N32      f<3>
N773      N17      f_sel<0>
N851      N16      f_sel<1>
N780      N9       func_sel<0>
N768      N20      func_sel<1>
N844      N24      func_sel<2>
N775      N0       gnd!
N847      N64      inv_r
N845      N67      inv_s
N778      N41      iq_master_en
N798      N54      iq_slave_en
N776      N69      ireg_a_wr
N823      N58      ireg_b_wr
N837      N37      ireg_wr
N817      N65      p<0>
N808      N68      p<1>
N802      N74      p<2>
N789      N35      p<3>
N816      N50      q0_in
N796      N44      q0_out
N790      N38      q3_in
N774      N2       q3_out
N791      N48      q_master_en
N800      N23      q_sel<0>
```

N787	N31	q_sel<1>
N850	N72	q_slave_en
N829	N70	r_sel<0>
N820	N36	r_sel<1>
N831	N60	reg_a_wr
N794	N51	reg_b_wr
N840	N59	reg_wr
N783	N6	s_sel<0>
N771	N7	s_sel<1>
N825	N56	select_a_hi<0>
N838	N47	select_a_hi<10>
N828	N55	select_a_hi<11>
N818	N53	select_a_hi<12>
N809	N5	select_a_hi<13>
N803	N25	select_a_hi<14>
N792	N14	select_a_hi<15>
N814	N30	select_a_hi<1>
N807	N12	select_a_hi<2>
N797	N19	select_a_hi<3>
N785	N61	select_a_hi<4>
N779	N33	select_a_hi<5>
N767	N39	select_a_hi<6>
N843	N13	select_a_hi<7>
N832	N63	select_a_hi<8>
N822	N27	select_a_hi<9>
N813	N87	select_b_hi<0>
N786	N77	select_b_hi<10>
N781	N76	select_b_hi<11>
N769	N49	select_b_hi<12>
N846	N3	select_b_hi<13>
N833	N21	select_b_hi<14>
N824	N46	select_b_hi<15>
N806	N86	select_b_hi<1>
N795	N85	select_b_hi<2>
N784	N84	select_b_hi<3>
N777	N83	select_b_hi<4>
N766	N82	select_b_hi<5>
N842	N81	select_b_hi<6>
N830	N80	select_b_hi<7>
N821	N79	select_b_hi<8>
N811	N78	select_b_hi<9>
N805	N1	vdd!
N819	N73	y<0>
N810	N75	y<1>
N804	N66	y<2>
N793	N26	y<3>
N799	N42	y_sel
N836	N28	zero

Devices in the netlist but not in the rules:

pmos nmos

The net-lists match.

	layout	schematic
	instances	
un-matched	0	0
rewired	0	0
size errors	0	0
pruned	0	0
active	1856	1856
total	1856	1856

si.out            Fri Apr 19 16:35:09 2019            3

	nets	
un-matched	0	0
merged	0	0
pruned	0	0
active	852	852
total	852	852

	terminals	
un-matched	0	0
matched but different type	0	0
total	86	86

Probe files from /home/grossfe2/ece425.work/LVS/schematic

devbad.out:

netbad.out:

mergenet.out:

termbad.out:

prunenet.out:

prunedev.out:

audit.out:

Probe files from /home/grossfe2/ece425.work/LVS/layout

devbad.out:

netbad.out:

mergenet.out:

termbad.out:

prunenet.out:

prunedev.out:

audit.out:

9. Difficulties in the design occurred numerous times while creating the datapath. Routing wires was often difficult due to there being so many elements to work with. Even routing through multiple layers was difficult. Getting sizing right was also a tough thing for the MP. Even now, my design is still larger than it should be but it was even larger before I tried working with it. Debugging the design was also a pain, specifically for the layout. It became very hard to track things in the layout view.

10. a) The distance between *vdd* and *gnd* varies in the design due to smaller modules being made from different sizes. However, the median measurement between the signals was roughly 3um. I didn't really choose to have it as 3um however it is good to keep the length of the design small because the width will be VERY long (mostly due to the regfile and ALU). Along with that, we have to stack multiple bitslices on top of each other which only increases the height, so its important to minimize that distance.

b) Gates can be sized differently for a variety of reasons (as told in the question). One possible reason is to deal with race conditions with the signals. Changing the sizing of the transistors can allow two signals (one of which may be travelling slower than the other) to arrive at the same time. For example, if you have an AND gate with one input coming from metal1 but the other coming from metal3. Clearly we need the metal3 signal to come faster (or slow down the metal1 signal) to avoid problems. Resizing accomplishing this.