

ALU Functions:

1. ADD:

Implemented by using the adder given. inv_r and inv_s are both set to high because they are active low. We want to add two positive numbers.

2. SUBR

Uses the adder from ADD but we have $inv_r = 0$ and $inv_s = 1$ and $C_{in} = 1$, giving us $S + (-R)$, where $(-R)$ is just the two's complement of R .

3. SUBS

Uses the adder from ADD but we have $inv_r = 0$ and $inv_s = 1$ and $C_{in} = 1$, giving us $S + (-R)$, where $(-R)$ is just the two's complement of R .

4. OR

We use the *logic* in our ALU to get the OR value. We have $inv_r = 0$ and $inv_s = 0$. We use DeMorgan's law to get $R \text{ OR } S$ from $\sim R \text{ NAND } \sim S$.

5. AND

We use the *logic* in our ALU to get the AND value. We have $inv_r = 0$ and $inv_s = 0$. We use DeMorgan's law to get $R \text{ AND } S$ from $\sim R \text{ NOR } \sim S$.

6. NOTRS


We use the same exact logic as the AND function but we set $inv_r = 1$ and keep $inv_s = 0$. This gives us $R \text{ NOTRS } S$ from $R \text{ NOR } \sim S$.

7. XOR

We use the XOR gate in the ALU logic to produce the XOR function. We set $inv_r = 1$ and $inv_s = 1$ to make sure our logic uses R and S .

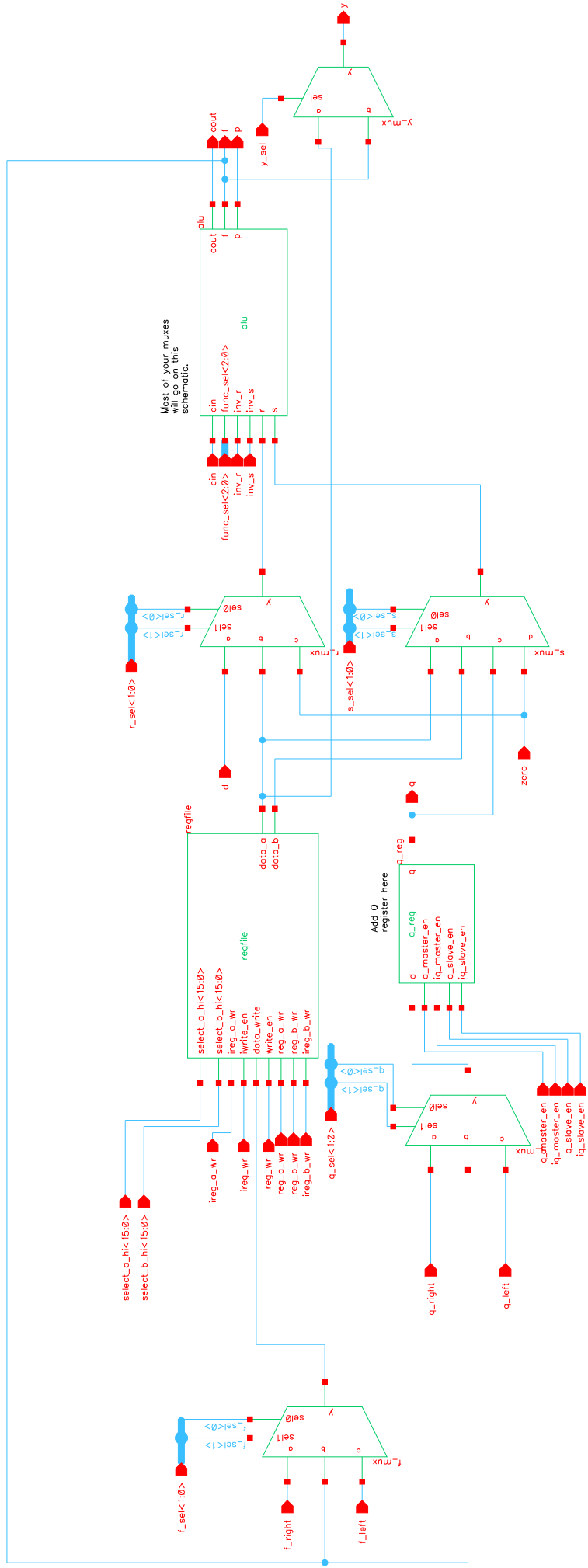8. XNOR

The XNOR function uses the exact same signals as XOR but we invert the output to get XNOR.



Page 1 of 1

